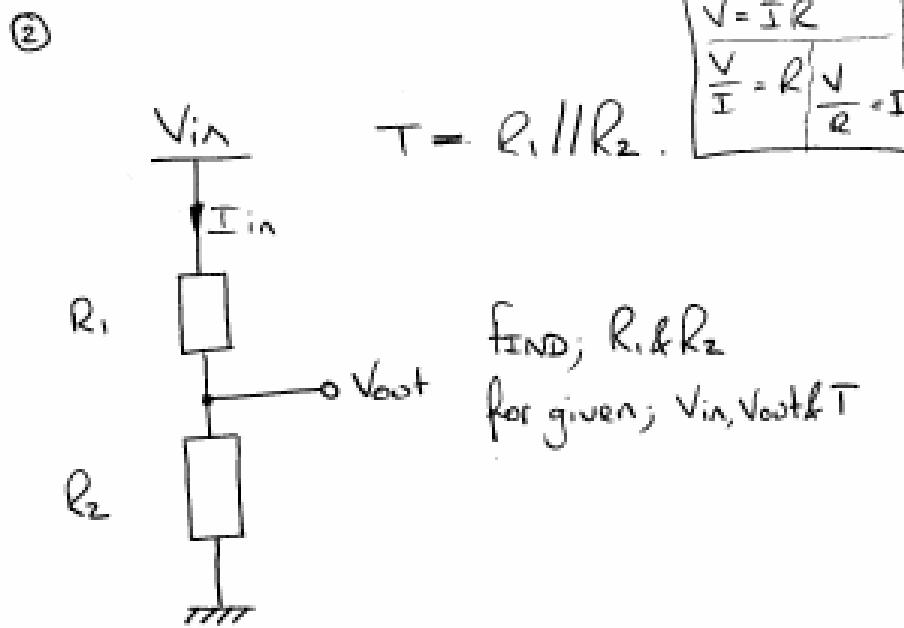


① To calculate resistor values for a voltage divider, where the impedance looking back into the divider is deterministic and independent of the divider value:



③ $I_{in} = \frac{V_{in}}{R_1 + R_2}$

⑤ $V_{out} = \frac{V_{in}}{R_1 + R_2} \cdot R_2$

④ $V_{out} = I_{in} \cdot R_2$

$V_{out} = \frac{V_{in} \cdot R_2}{R_1 + R_2}$

$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$

$\frac{V_{in}}{V_{out}} = \frac{R_1 + R_2}{R_2} = \frac{R_1}{R_2} + \frac{R_2}{R_2}$

$\frac{V_{in}}{V_{out}} = \frac{R_1}{R_2} + 1$

⑥ $R_1 \parallel R_2 = \frac{R_1 \cdot R_2}{R_1 + R_2}$

$T = \frac{R_1 \cdot R_2}{R_1 + R_2}$

$\frac{1}{T} = \frac{R_1 + R_2}{R_1 \cdot R_2}$

$= \frac{R_1}{R_1 \cdot R_2} + \frac{R_2}{R_1 \cdot R_2}$

$= \frac{1}{R_2} + \frac{1}{R_1}$

$\frac{1}{T} - \frac{1}{R_1} = \frac{1}{R_2}$

$R_2 = \frac{1}{\frac{1}{T} - \frac{1}{R_1}}$

$R_2 = \frac{R_1 \cdot T}{R_1 - T} \leftarrow \underline{\underline{A}}$

①

$$\frac{V_{in}}{V_{out}} = \frac{R_1}{R_2} + 1$$

$$\frac{V_{in}}{V_{out}} - 1 = \frac{R_1}{R_2}$$

$$\left(\frac{V_{in}}{V_{out}} - 1\right) R_2 = R_1$$

$$R_2 = \frac{R_1 \cdot T}{R_1 - T}$$

$$\left(\frac{V_{in}}{V_{out}} - 1\right) \left(\frac{R_1 \cdot T}{R_1 - T}\right) = R_1$$

$$\frac{V_{in} \cdot R_1 \cdot T}{V_{out} (R_1 - T)} - \frac{R_1 \cdot T}{R_1 - T} = R_1$$

$$\frac{V_{in} \cdot R_1 \cdot T}{V_{out} \cdot R_1 - V_{out} \cdot T} - \frac{R_1 \cdot T}{R_1 - T} = R_1$$

$$\frac{V_{in} \cdot T}{V_{out} \cdot R_1 - V_{out} \cdot T} - \frac{T}{R_1 - T} = 1$$

$$\frac{(R_1 - T) \cdot V_{in} \cdot T - (V_{out} \cdot R_1 - V_{out} \cdot T) T}{(R_1 - T) (V_{out} \cdot R_1 - V_{out} \cdot T)} = 1$$

$$\frac{A}{B} = 1$$

$$A = V_{in} \cdot T \cdot R_1 - V_{in} \cdot T^2 - \cancel{V_{out} \cdot T \cdot R_1} + \cancel{V_{out} \cdot T^2}$$

$$B = V_{out} \cdot R_1^2 - \cancel{V_{out} \cdot T \cdot R_1} - \cancel{V_{out} \cdot T \cdot R_1} + \cancel{V_{out} \cdot T^2} \\ = V_{out} \cdot R_1^2 - 2V_{out} \cdot T \cdot R_1 + V_{out} \cdot T^2$$

②

$$\frac{-V_{in} \cdot T^2 + V_{in} \cdot T \cdot R_1}{V_{out} \cdot R_1^2 - V_{out} \cdot T \cdot R_1} = 1$$

$$\frac{T(-V_{in} \cdot T + V_{in} \cdot R_1)}{R_1(V_{out} \cdot R_1 - V_{out} \cdot T)} = 1$$

$$\frac{-V_{in} \cdot T + V_{in} \cdot R_1}{V_{out} \cdot R_1 - V_{out} \cdot T} = \frac{R_1}{T}$$

$$\frac{V_{in}(-T + R_1)}{V_{out}(-T + R_1)} = \frac{R_1}{T}$$

$$\frac{V_{in}}{V_{out}} = \frac{R_1}{T}$$

$$\boxed{\frac{V_{in} T}{V_{out}} = R_1} \iff \underline{\underline{B}}$$

$$R_1 = \frac{V_{in} T}{V_{out}}$$

$$R_2 = \frac{R_1 \cdot T}{R_1 - T}$$